

--	--	--	--	--	--	--	--	--	--

VIGNAN'S INSTITUTE OF MANAGEMENT AND TECHNOLOGY FOR WOMEN
(An Autonomous Institution)

I-B.Tech.-I-Semester Regular Examinations, February-2025

BASIC ELECTRICAL ENGINEERING
(Common to CSE (DS and IT))

Time: 3 Hours

Max. Marks: 60

(Answer All Questions)

Note: Question paper consists of Part-A & Part-B.

- **Part-A** for 10M, ii) **Part-B** for 50marks
- **Part A** is compulsory, consists of 10 sub questions from all units carrying equal marks.
- **Part-B** consists of **10 questions** (numbered from 2 to 11) carrying **10marks** each. From each unit there are 2 questions and the students should answer one of them. Hence the student should answer **5 questions** from **Part-B**.

PART-A


(10Marks)

- 1 a. State KCL 1M
- 1 b. Write the time constant of RL and RC circuits 1M
- 1 c. Define form factor 1M
- 1 d. The apparent power in RC circuit is 150VA and active power is 100W calculate power factor 1M
- 1 e. Define autotransformer 1M
- 1 f. Define efficiency of transformer 1M
- 1 g. Define a generator 1M
- 1 h. Write the formula for synchronous speed w.r.to frequency and number of poles 1M
- 1 i. Write the full forms of MCB, ELCB 1M
- 1 j. What is the need of earthing 1M

PART-B

(50Marks)

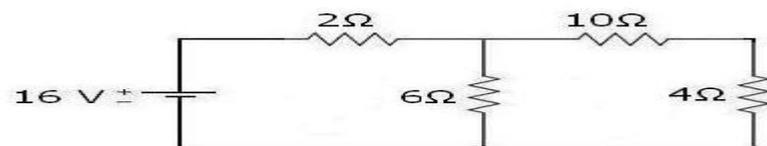- 2 a Obtain an expression for transient current flowing through R-L series circuit excited by D.C source at $t= 0+$. **5M**
 - 2 b State and explain superposition theorem **5M**
- OR
- 3 Find the current in 4Ω resistor using thevenin's theorem **10 M**



- 4 a Define cycle, amplitude, RMS value ,average value **5M**
 - 4 b A series circuit consisting of a 10Ω resistor and 10 mH inductance is driven by a 50Hz ac voltage source of maximum value 100V find the equivalent impedance and current flowing in the circuit **5M**
- OR
- 5 Obtain an expression for active, reactive and complex power in a single-phase series RLC circuit excited by sinusoidal voltage and also **10M**

draw the power triangle for RLC circuit

- 6 a Derive the EMF equation of transformer. **5M**
6 b Compare the autotransformer and transformer and list the advantage of autotransformer over two winding transformer **5M**
OR
- 7 Explain the construction and working principle of a transformer **10M**
- 8 a Explain the construction and working of a DC generator **5M**
8 b A 6 pole 50 HZ supply of induction motor has a full load speed of 970 rpm find the full load slip and rotor frequency **5M**
OR
- 9 Explain the construction details of synchronous generator **10M**
- 10 a What are batteries? How are they classified **5M**
10 b Calculate the total energy consumed per day (in terms of units) using following loads: i) 6 number of 50W bulbs operated 6 hours per day
ii) 736W motor operating 1 hour per day **5M**
iii) 1000W heater operated 1 hour per day
OR
- 11 Explain in detail the types of wires and cables? **10M**

*****VMTW*****